

# Module 1, Assignment 2

---

## Contents

<b>1</b>	<b>Goal of the Assignment</b>	<b>1</b>
<b>2</b>	<b>Task Description</b>	<b>1</b>
2.1	Implement a Generic NAND Gate . . . . .	1
2.2	Simulate the Design . . . . .	3
2.3	Synthesize the Design . . . . .	3
2.4	Implement the Design, Generate the Bitstream, and Program the FPGA . . . . .	5

---

## 1 Goal of the Assignment

In this assignment, you will implement a generic NAND gate in VHDL. You will investigate the elaborated design, i.e., the representation of the design with generic components, and the technology-mapped design, i.e., the design mapped to device-specific primitives.

## 2 Task Description

### 2.1 Implement a Generic NAND Gate

In Task 1, you have implemented an AND gate with two registered inputs and one registered output. Now, your task is to implement a generic NAND gate with registered inputs and a registered output. The inputs to the NAND gate are the 16 switches of the Nexys board, i.e., a 16-bit logic vector. The output will be assigned to LED 0 on the Nexys board. Use the constraints file (*constr\_Nexys\_A7.xdc*) provided in PANDA to assign the pins of your block design to the correct pins of the FPGA package. The NAND gate will evaluate the logic function:

$$f(x_0, x_1, \dots, x_{N-1}) = \overline{x_0 \wedge x_1 \wedge \dots \wedge x_{N-1}} \quad 2 \leq N \leq 16 \quad (1)$$

In other words, implement a module which performs a logical NAND on the  $N$  LSBs of the input vector and provides the result at its output. Make  $N$  a configurable parameter in your VHDL code.

*Hint: To make your design generic, you could, for example, use the for-generate statement.*


For the following schematics, assume gates with two inputs to be used by Vivado.

Draw the schematic you expect for the elaborated design with  $N = 4$ :



How many logical gates are you expecting to be used with  $N = 4$ ? 4

 Draw the schematic you expect for the elaborated design with  $N = 7$ :



How many logical gates are you expecting to be used with  $N = 7$ ? 7

Draw the schematic you expect for the elaborated design with  $N = 16$ :

How many logical gates are you expecting to be used with  $N = 16$ ? 16

Verify the correctness of your design by comparing your expected schematic to the schematic generated by Vivado. Do you see structural differences in the schematics? If yes, why?

## 2.2 Simulate the Design

Create a test bench and verify the design's correctness with a behavioral simulation.

## 2.3 Synthesize the Design

Determine the parameter  $K$  (#inputs per LUT) for the LUTs used in the FPGA of the Nexys board: \_\_\_\_\_

Draw the schematic you expect for the synthesized design with  $N = 4$ :

How many LUTs are you expecting to be used with  $N = 4$ ? 1

Draw the schematic you expect for the synthesized design with  $N = 7$ :

How many LUTs are you expecting to be used with  $N = 7$ ? 2

Draw the schematic you expect for the synthesized design with  $N = 16$ :



How many LUTs are you expecting to be used with  $N = 16$ ? 3

Synthesize the design and compare your schematic to the schematic after synthesis. Do the schematics differ from each other? If yes, why?

---

---

---

---

## 2.4 Implement the Design, Generate the Bitstream, and Program the FPGA

Implement the design, generate the bitstream, program the FPGA, and test your design on the hardware.